 


# **REGISTER TRANSFER AND MICROOPERATIONS**

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Arithmetic Microoperations**
- **Logic Microoperations**
- **Shift Microoperations**
- **Arithmetic Logic Shift Unit**

# MICROOPERATION

An elementary operation performed during one clock pulse, on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

f: shift, count, clear, load, add,...

# REGISTER TRANSFER LANGUAGE

**Definition of the (internal) organization of a computer**

- **Set of registers and their functions**
- **Microoperations Set**
  - Set of allowable microoperations provided by the organization of the computer**
- **Control signals that initiate the sequence of microoperations**

**For any function of the computer, a sequence of microoperations is used to describe it**

**----> *Register transfer language***

- **A symbolic language**
- **Used to describe the microoperation transfers among registers**

# REGISTER TRANSFER

**Designation of a register** - a register  
 - portion of a register  
 - a bit of a register



**Common ways of drawing the block diagram of a register**

Register



Numbering of bits

Showing individual bits

  

Subfields

**Representation of a transfer(parallel)**

$R2 \leftarrow R1$

A simultaneous transfer of all bits from the source to the destination register, during one clock pulse

**Representation of a controlled(conditional) transfer**

P:  $R2 \leftarrow R1$

A binary condition( $p=1$ ) which determines when the transfer is to occur


If ( $p=1$ ) then ( $R2 \leftarrow R1$ )

# HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


## Implementation of controlled transfer

P:  $R2 \leftarrow R1$

### Block diagram

 

### Timing diagram

 



## Basic Symbols for Register Transfers

Symbols	Description	Meaning
Capital letters and numerals	Denotes a register	MAR, R2
Parentheses ( )	Denotes a part of a register	R2(0-7), R2(L)
Arrow $\leftarrow$	Denotes transfer of information	$R2 \leftarrow R1$
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	$A \leftarrow B, B \leftarrow A$

 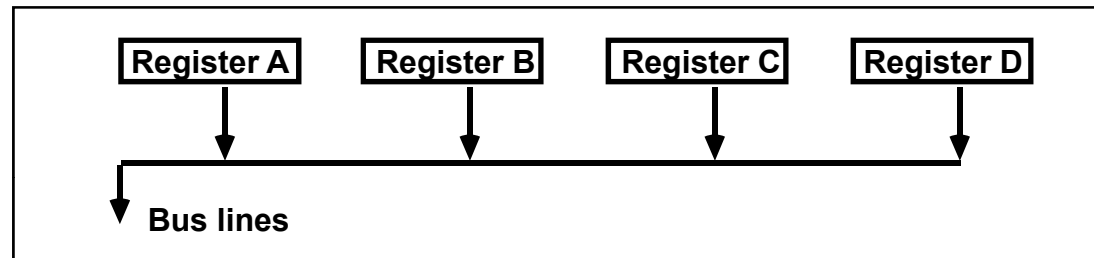
# BUS AND MEMORY TRANSFER

Bus is a path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations.


From a register to bus:  $BUS \leftarrow R$



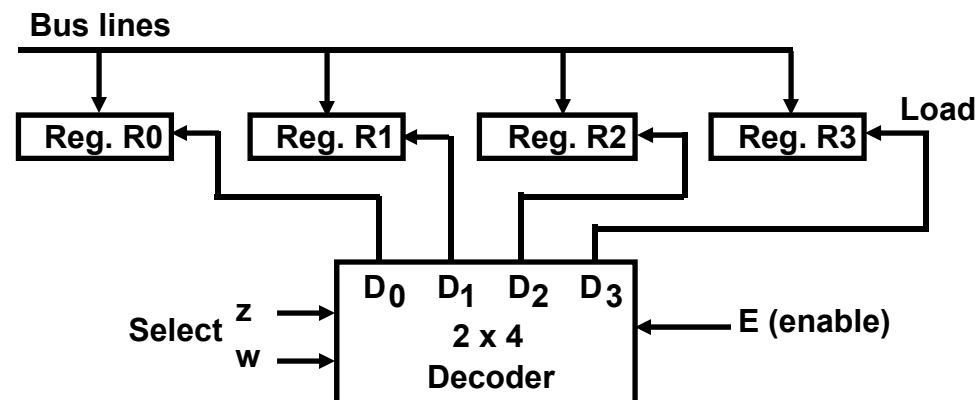
# TRANSFER FROM BUS TO A DESTINATION REGISTER




## Three-State Bus Buffers

 

## Bus line with three-state buffers

 

# MEMORY TRANSFERS

 

**Memory read** micro-op:  $DR \leftarrow M$

**Memory write** micro-op:  $M \leftarrow DR$

or (  $DR \leftarrow M[AR]$  )

or (  $M[AR] \leftarrow DR$  )



# ARITHMETIC MICROOPERATIONS

## Four types of microoperations


- Register transfer microoperations
- Arithmetic microoperations
- Logic microoperations
- Shift microoperations

## \* Summary of Arithmetic Micro-Operations


$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

# BINARY ADDER


## Binary Adder

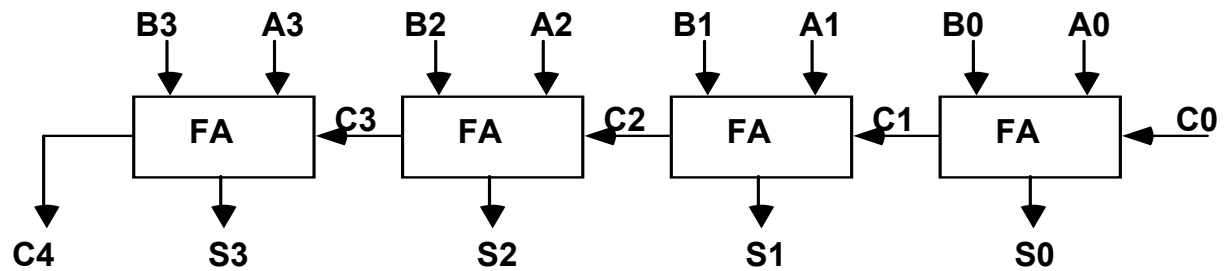


## Binary Adder-Subtractor

 

## Binary Incrementer

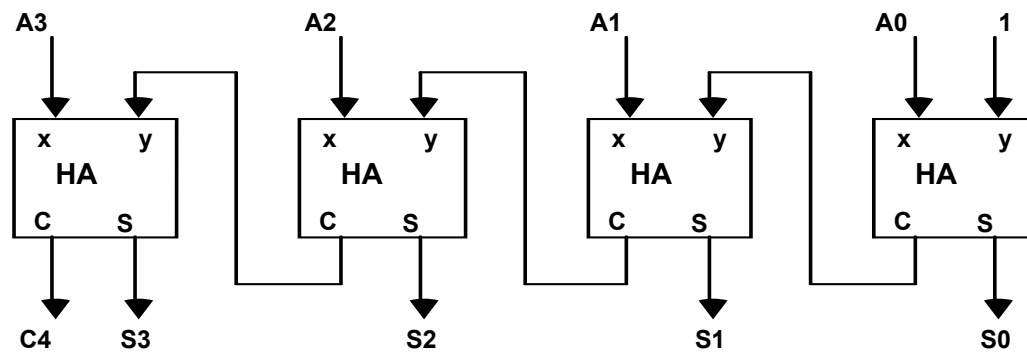

# ARITHMETIC CIRCUIT

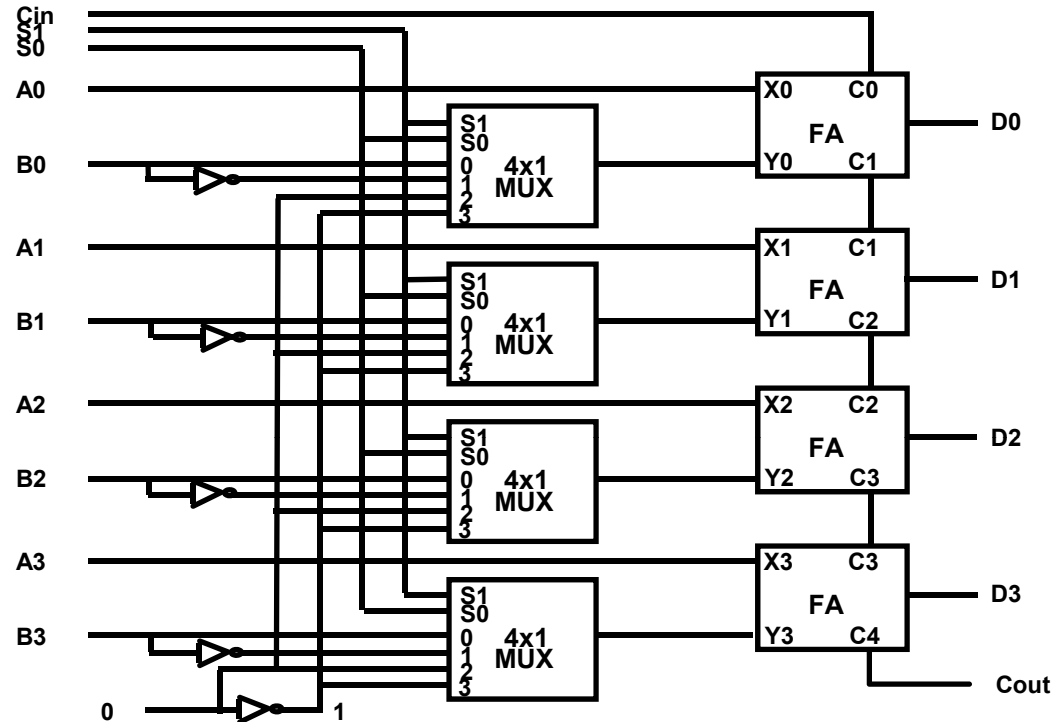

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

# LOGIC MICROOPERATIONS

Specify binary operations on the strings of bits in registers.

- useful for bit manipulations on binary data

**AND:** Mask out certain group of bits

**OR :** Merge binary or character data

- useful for making logical decisions based on the bit value

## Applications

Manipulating individual bits or a field(portion) of a word in a register


- |                        |                   |
|------------------------|-------------------|
| - Selective-set        | $A + B$           |
| - Selective-complement | $A \oplus B$      |
| - Selective-clear      | $A \cdot \bar{B}$ |
| - Mask (Delete)        | $A \cdot B$       |
| - Insert               | $(A \cdot B) + C$ |
| - Compare              | $A \oplus B$      |
| - Packing              | $(A \cdot B) + C$ |
| - Unpacking            | $A \cdot B$       |

# LIST OF LOGIC MICROOPERATIONS

- List of Logic Micro-Operations
  - 16 different logic operations with 2 binary vars.
  - n binary vars  $\rightarrow 2^2^n$  functions
- Truth tables for 16 functions of 2 variables and the corresponding 16 logic micro-operations

x	0 0 1 1	<i>Boolean Function</i>	<i>Micro-Operations</i>	<i>Name</i>
y	0 1 0 1			
	0 0 0 0	$F_0 = 0$	$F \leftarrow 0$	Clear
	0 0 0 1	$F_1 = xy$	$F \leftarrow A \wedge B$	AND
	0 0 1 0	$F_2 = xy'$	$F \leftarrow A \wedge B'$	Transfer A
	0 0 1 1	$F_3 = x$	$F \leftarrow A$	
	0 1 0 0	$F_4 = x'y$	$F \leftarrow A' \wedge B$	Transfer B
	0 1 0 1	$F_5 = y$	$F \leftarrow B$	
	0 1 1 0	$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Exclusive-OR
	0 1 1 1	$F_7 = x + y$	$F \leftarrow A \vee B$	OR
	1 0 0 0	$F_8 = (x + y)'$	$F \leftarrow (A \vee B)'$	NOR
	1 0 0 1	$F_9 = (x \oplus y)'$	$F \leftarrow (A \oplus B)'$	Exclusive-NOR
	1 0 1 0	$F_{10} = y'$	$F \leftarrow B'$	Complement B
	1 0 1 1	$F_{11} = x + y'$	$F \leftarrow A \vee B$	Complement A
	1 1 0 0	$F_{12} = x'$	$F \leftarrow A'$	
	1 1 0 1	$F_{13} = x' + y$	$F \leftarrow A' \vee B$	NAND
	1 1 1 0	$F_{14} = (xy)'$	$F \leftarrow (A \wedge B)'$	
	1 1 1 1	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's
 
# HARDWARE IMPLEMENTATION OF LOGIC MICROOPERATIONS



Function table

$S_1$	$S_0$	Output	$\mu$ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

# SHIFT MICROOPERATIONS

## Shifts


- **Logical shift** : shift in a 0 into the extreme flip-flop
- **Circular shift** : circulates the bits of the register around the two ends
- **Arithmetic shift** : shifts a signed number (shift with sign extension)

Left shift -> multiplied by 2

Right shift -> divided by 2

## Arithmetic shifts for signed binary numbers


- Arithmetic shift-right

 

- Arithmetic shift-left Overflow V may occur


## Shift Micro-Operations

<i>Symbol</i>	<i>Description</i>
$R \leftarrow \text{shl } R$	Shift-left register R
$R \leftarrow \text{shr } R$	Shift-right register R
$R \leftarrow \text{cil } R$	Circular shift-left register R
$R \leftarrow \text{cir } R$	Circular right-shift register R
$R \leftarrow \text{ashl } R$	Arithmetic shift-left register R
$R \leftarrow \text{ashr } R$	Arithmetic shift-right register R

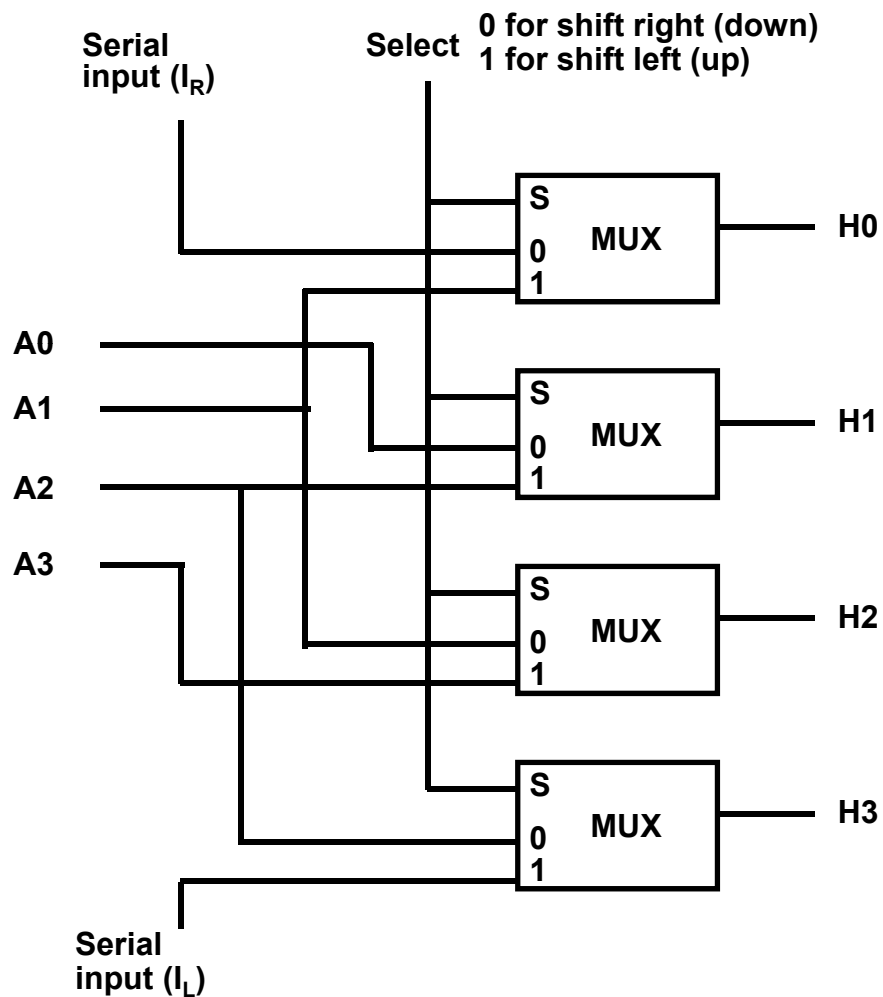**HARDWARE IMPLEMENTATION OF SHIFT MICROOPERATIONS**



# ARITHMETIC LOGIC SHIFT UNIT

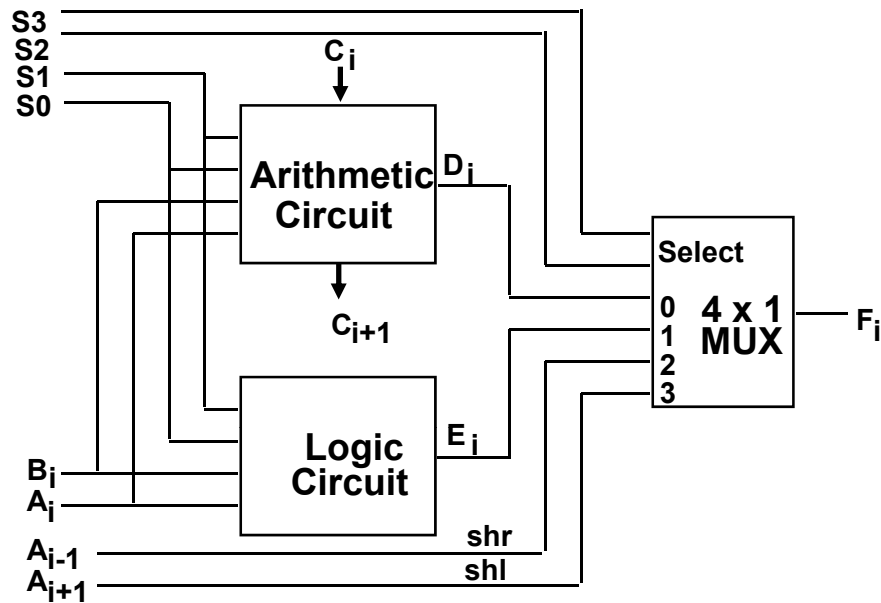

S3	S2	S1	S0	Cin	Operation	Function
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement A
1	0	X	X	X	$F = shr A$	Shift right A into F
1	1	X	X	X	$F = shl A$	Shift left A into F